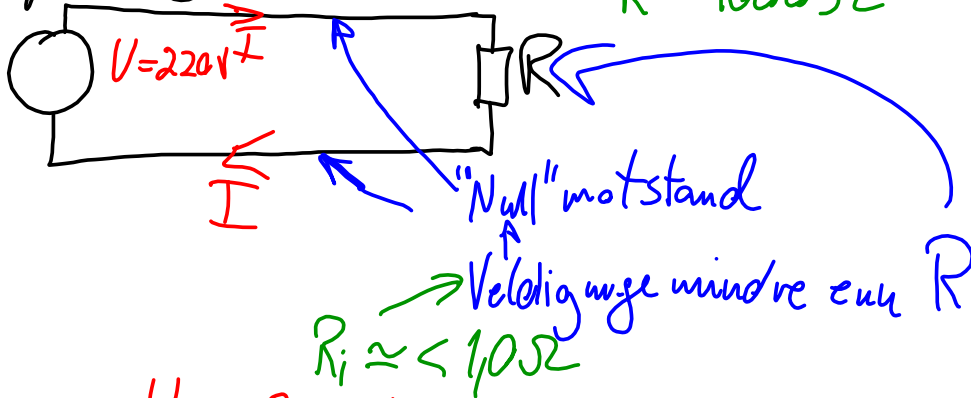


Spenningskilde




$$I = \frac{U}{R} = \frac{220 \text{ V}}{1000 \Omega} = 0,220 \text{ A} = 220 \text{ mA}$$

med R_i

Ekvivalent skjema

$$R_i = 1,0 \Omega$$

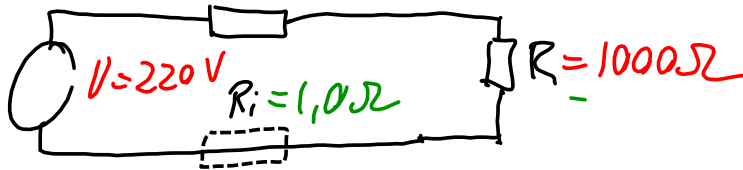

$$I = \frac{U}{R_T} = \frac{220 \text{ V}}{R + R_i + R_i} = \frac{220 \text{ V}}{(1000 + 2,0) \Omega} = \frac{220 \text{ V}}{1002 \Omega}$$


Hvordan regne ut den indre motstand i ledningene R_i

R_i bør være minst mulig for at ilde ledningene skal bli for varme

↳ Strømstyrken bestemmer det

"Bli for varm": (Eks med motstand)

Effekt: P_R

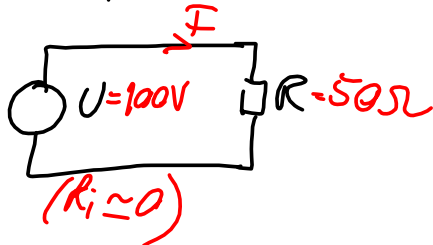

$$I = \frac{U}{R} = \frac{100V}{50\Omega} = 2,0 A$$

$$P_R = U \cdot I = 100V \cdot 2,0A = 200 W$$

↑ Effekt ← spenning → strøm

$$\text{Energj} = P_R \cdot t$$

$$\text{Eks: } t = 10 s$$

$$E = P_R \cdot t = 200 [W] \cdot 10 [s] = 2000 [W \cdot s]$$

↑ Joule
↑ Effekt ← spenning → strøm

symbol for varme: energy
↑ Varme

$$Q = c \cdot m \cdot \Delta t$$

↑ Spesifikk varmekapasitet
(avhengig av materialet)
↳ finnes i tabeller

↑ massen ← temp. økning





$$\Delta t = \frac{Q}{c \cdot m} = \frac{2000 [J]}{0,51 \left[\frac{kJ}{kg \cdot K} \right] \cdot 0,1 [kg]} = \frac{2,0 [kJ]}{0,051 \left[\frac{kJ}{kg \cdot K} \right]}$$

$$= 39,2 [K]$$

↑ Kelvin (temp.)

Spennning U [V]



V ← symbol for spennning (i USA)

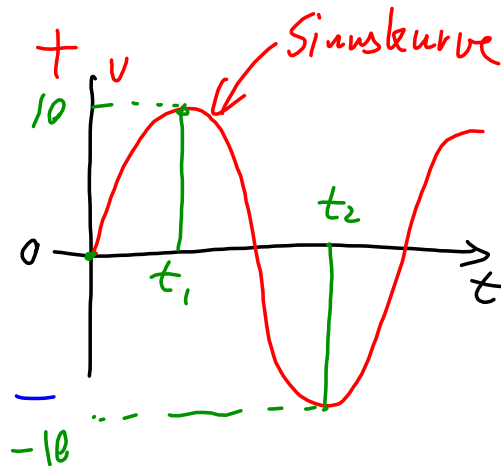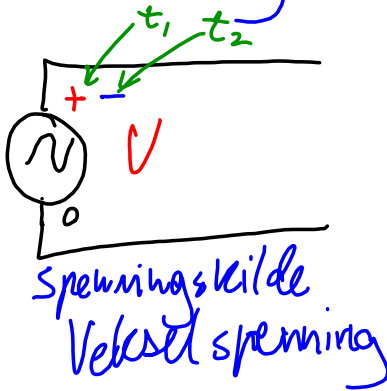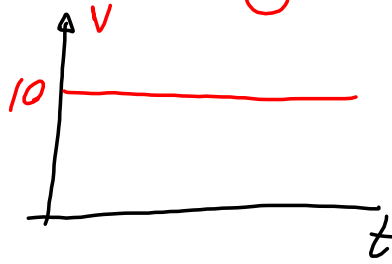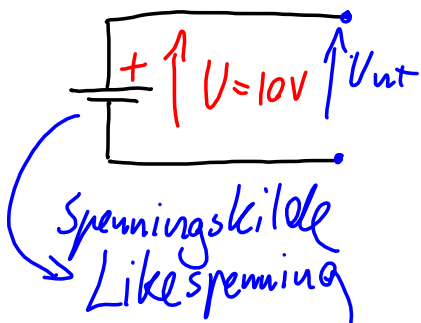

$$u(t) = a \cdot \sin 2\pi f t = a \sin 2\pi \frac{t}{T}$$

$$t = T : a \cdot \sin 2\pi \frac{T}{T} = a \cdot \sin 2\pi$$
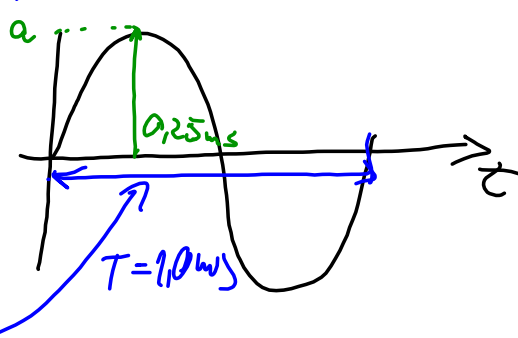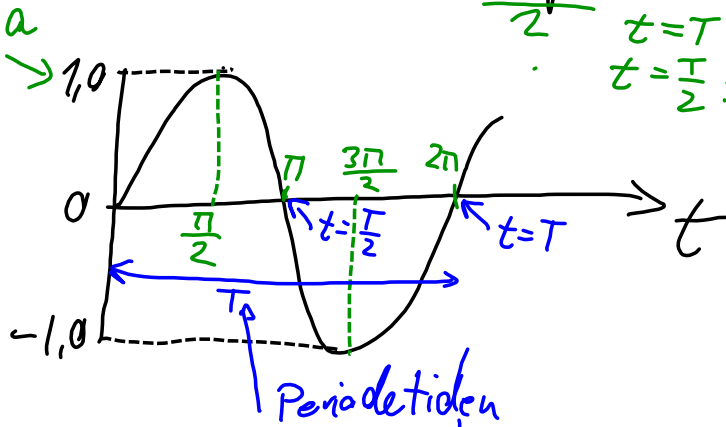
$$t = \frac{T}{2} : a \cdot \sin 2\pi \frac{\frac{T}{2}}{T} = a \cdot \sin \pi$$



$$f = 1000 \text{ Hz}$$

$$T = \frac{1}{f} = \frac{1}{1000} [\text{s}]$$

$$= 0,001 \text{ s} = 1 \text{ ms}$$

$$u(t) = a \cdot \sin 2\pi \cdot 1000 \cdot 0,25 \frac{1}{10^3}$$

$$= a \cdot \sin 2\pi \cdot 0,25 =$$

$$a \cdot \sin 2\pi \frac{1}{4} = a \cdot \sin \frac{\pi}{2}$$

