
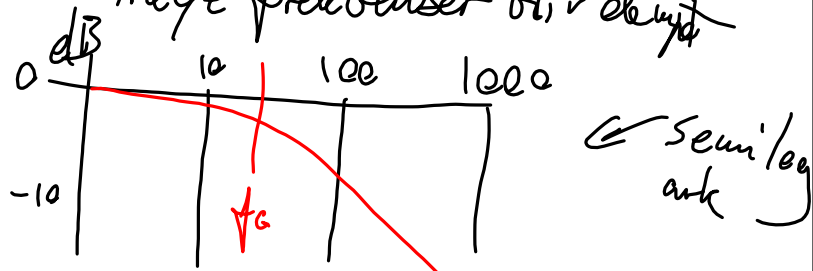


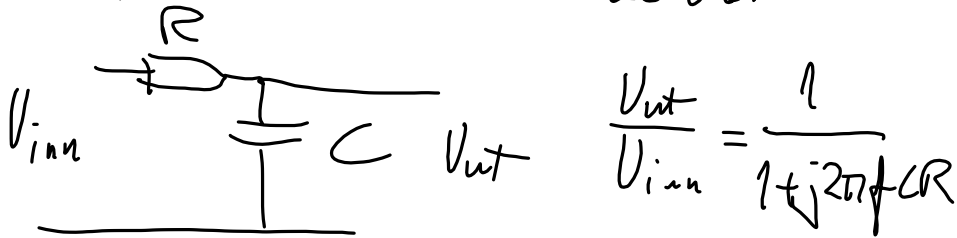
LP-filter \rightarrow Low frekvenser slipper igjennom
 Høye frekvenser blir dempet



LP-filter med kondensator



LP-filter med induktanse

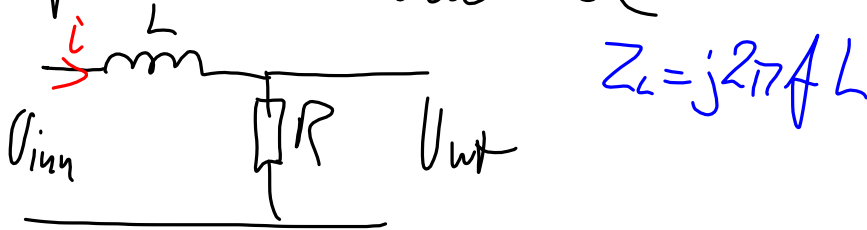

$$i = \frac{V_{inn}}{R + j2\pi fL} \quad V_{ut} = i \cdot R$$

$$V_{ut} = \frac{V_{inn}}{R + j2\pi fL} \cdot R$$

$$\frac{V_{ut}}{V_{inn}} = \frac{R}{R + j2\pi fL} = \frac{1}{1 + j2\pi f \frac{L}{R}}$$

$$1 = 2\pi f \cdot \frac{L}{R}$$

$$f_g = \frac{1}{2\pi} \frac{L}{R} = \frac{R}{2\pi L}$$


HP-filter (High Pass filter)

Bruk 1: Hvis ditt signal har en


DC-komponent som vi ikke ønsker



Bruk 2

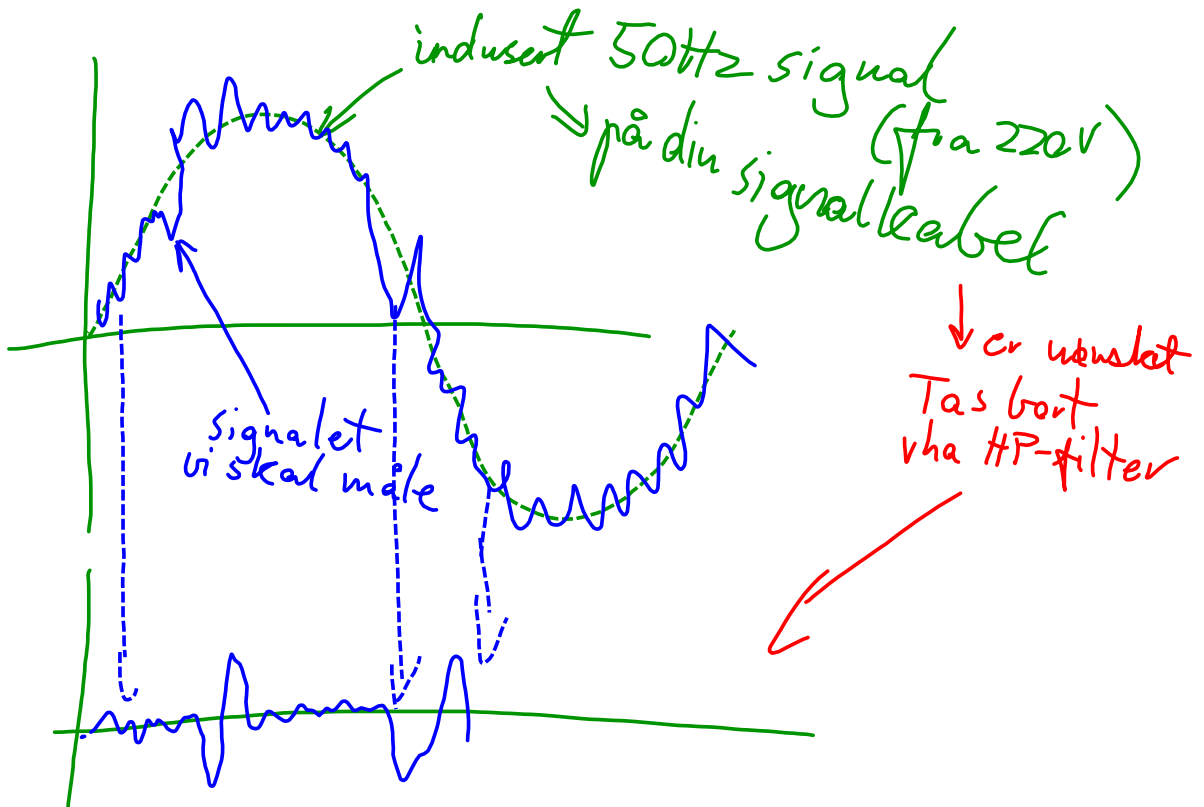

HP-filter vha spole

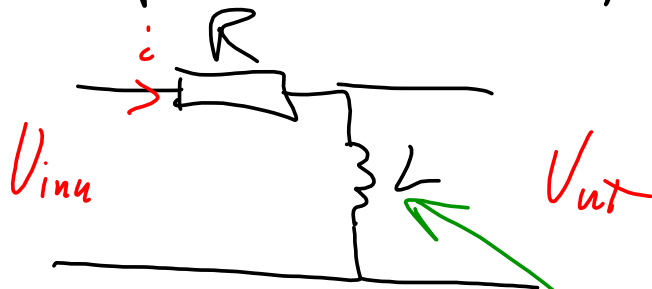

$$i = \frac{V_{inu}}{R + Z_L} \quad V_{ut} = i \cdot Z_L$$

$$Z_L = j2\pi f L$$

$$V_{ut} = \frac{V_{inu} \cdot Z_L}{R + Z_L}$$

$$\frac{V_{ut}}{V_{inu}} = \frac{Z_L}{R + Z_L} = \frac{j2\pi f L}{R + j2\pi f L} = \frac{j2\pi f \frac{L}{R}}{1 + j2\pi f \frac{L}{R}}$$


$$\frac{V_{ut}}{V_{inu}} = \frac{j \frac{f}{f_0}}{1 + j \frac{f}{f_0}}$$

HP-filter $f_0 = \frac{1}{2\pi f_0 \frac{L}{R}}$

$$f_0 = \frac{1}{2\pi \frac{L}{R}}$$

LP-filter
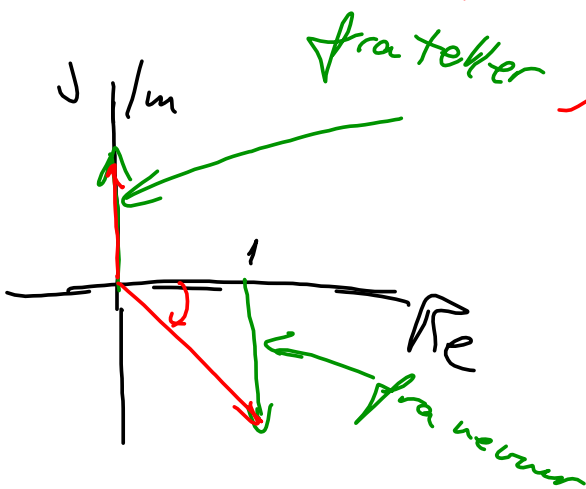
$$\frac{V_{ut}}{V_{inu}} = \frac{1}{1 + j \frac{f}{f_0}}$$



HP-filter vha C (kondensator)



$$i = \frac{V_{in}}{Z_C + R} \quad U_{out} = i \cdot R$$

$$U_{out} = \frac{V_{in}}{Z_C + R} \cdot R$$


$$\frac{U_{out}}{V_{in}} = \frac{R}{Z_C + R} = \frac{R}{\frac{1}{j2\pi f C} + R} = \frac{j2\pi f C R}{1 + j2\pi f C R}$$

$$1 = 2\pi f_g C R$$


$$f_g = \frac{1}{2\pi C R}$$


$$\frac{U_{in}}{U_{out}} = \frac{j \frac{f}{f_g}}{1 + j \frac{f}{f_g}}$$

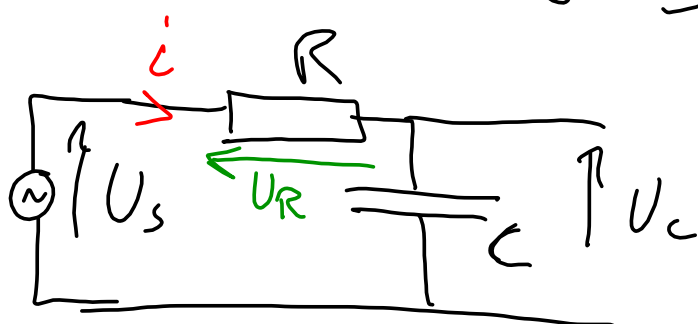Hvordan er spenninger og strøm i LP vha C



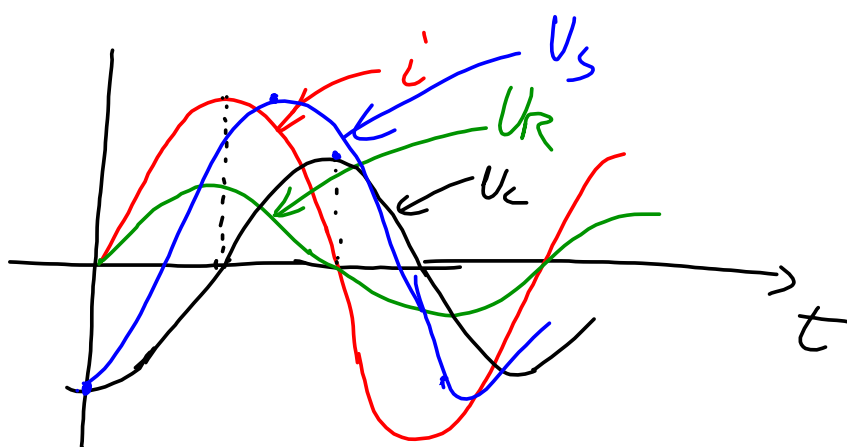
$$U_s = U_R + U_C$$
$$i = C \cdot \frac{dU}{dt}$$



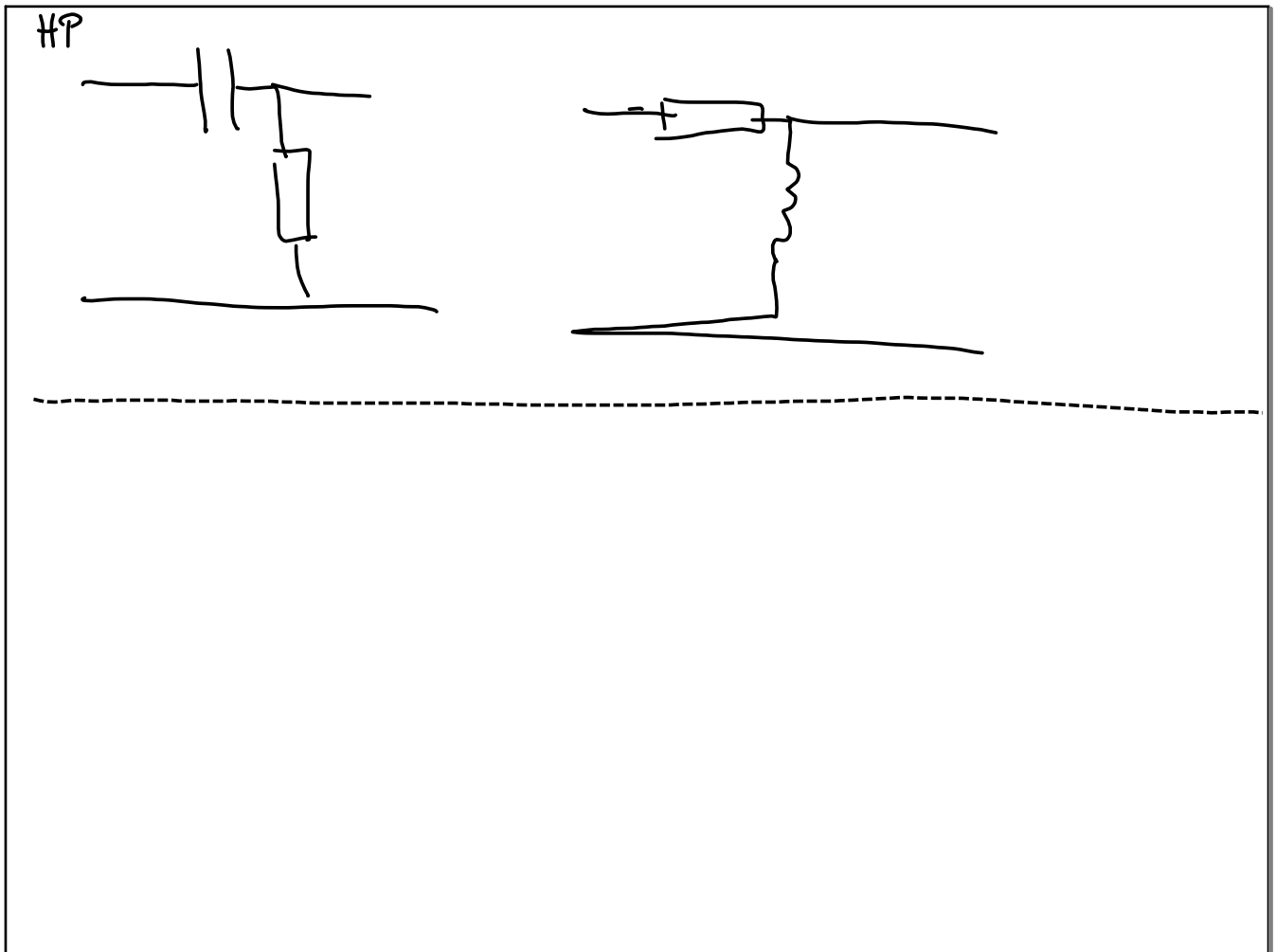

Seriekobling av spoler

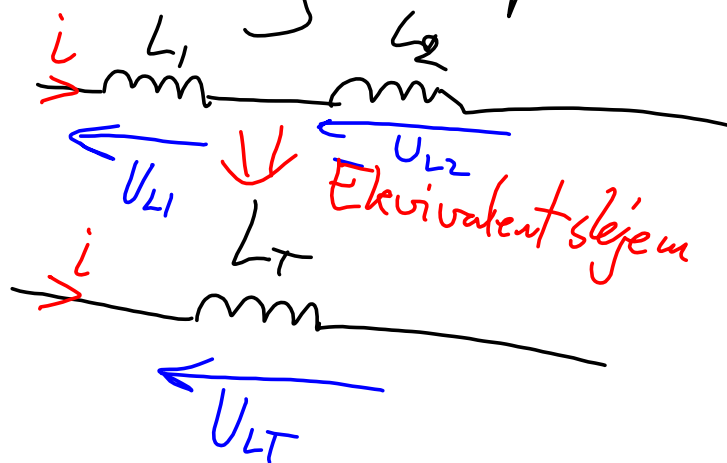

$$u = L \cdot \frac{di}{dt}$$

$$U_{LT} = U_{L1} + U_{L2}$$


$$L_T \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$

$$L_T = L_1 + L_2$$

$$U_{L1} = L_1 \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{U_{L1}}{L_1}$$

Parallellkobling av spoler

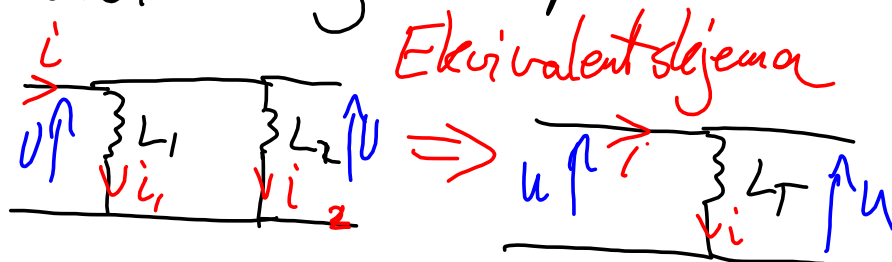

$$U = L_T \frac{d(i_1 + i_2)}{dt} = L_T \left(\frac{di_1}{dt} + \frac{di_2}{dt} \right)$$

$$U = L_T \left(\frac{U}{L_1} + \frac{U}{L_2} \right)$$

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2}$$