

$$U_1 - U_{R1} - U_2 = 0 \quad \leftarrow \text{Kirchoffs spenningslov}$$

$$U_1 = U_{R1} + U_2$$

$$U_1 = I \cdot R_1 + I \cdot R_2 = I (R_1 + R_2)$$

$$I = \frac{U_1}{R_1 + R_2} = \frac{5,0 [\text{V}]}{1500 [\Omega] + 2000 [\Omega]} = \frac{5,0 [\text{V}]}{3500 [\Omega]}$$

$$= 1,43 \cdot 10^{-3} [\text{A}] = 1,43 [\text{mA}]$$


$\uparrow$   
m

$$U_2 = I \cdot R_2 = 1,43 \cdot 10^{-3} [\text{A}] \cdot 2000 [\Omega]$$


$$= 1,43 \cdot 10^{-3} \cdot 2,0 \cdot 10^3 [\text{V}]$$

$$= 1,43 \cdot 2,0 [\text{V}] = 2,86 [\text{V}]$$


Ekvivalent skjema

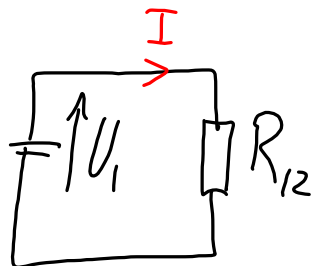

$$I = \frac{U_1}{R_{12}}$$

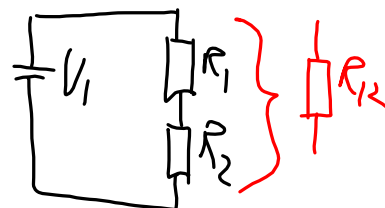

$$R_{12} = R_1 + R_2$$


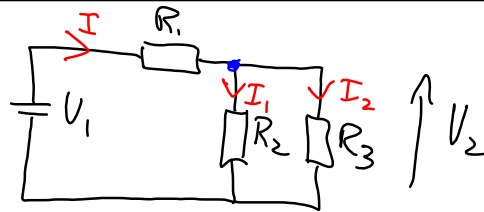


$$I - I_1 - I_2 = 0$$

Kirchoff's  
strømløse

$$I = I_1 + I_2$$

Ekvivalent skjema

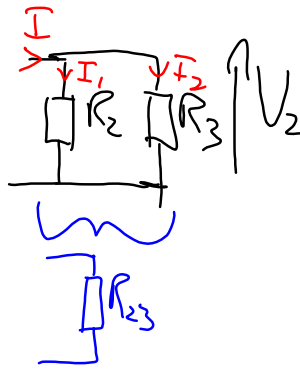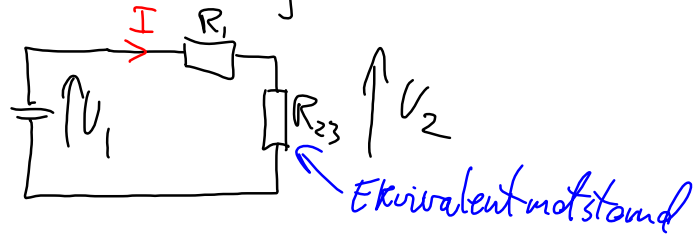

$$I = I_1 + I_2$$

$$\frac{U_2}{R_{23}} = \frac{U_2}{R_2} + \frac{U_2}{R_3}$$

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{R_3}{R_2 \cdot R_3} + \frac{R_2}{R_2 \cdot R_3} = \frac{R_3 + R_2}{R_2 \cdot R_3}$$

$$\frac{R_2 \cdot R_3}{R_{23}} = R_3 + R_2$$

$$R_2 \cdot R_3 = (R_3 + R_2) \cdot R_{23}$$

$$\frac{R_2 \cdot R_3}{R_3 + R_2} = R_{23}$$


← Parallell kobling  
av  $R_2$  og  $R_3$

$$I = \frac{U_1}{R_1 + R_{23}}$$

Effekt

Symbol:  $P$   
Bemærkelsen [W]


$$P = U \cdot I$$

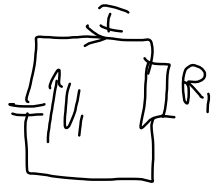

$$U_1 = 10,0 \text{ V} \quad R_1 = 5,0 \Omega$$

$$I = \frac{U_1}{R_1} = \frac{10,0 \text{ [V]}}{5,0 \text{ [\Omega]}} = 2,0 \text{ [A]}$$
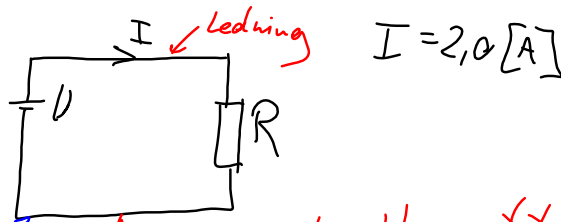
$$P = U \cdot I = 10,0 \text{ [V]} \cdot 2,0 \text{ [A]} = 20,0 \text{ [W]}$$




$$I = 2,0 \text{ [A]}$$

$$\frac{300 \text{ m}}{1,5 \text{ [m}^2\text{]}}$$

 $\uparrow$  ledning  $\rightarrow$  veldig liten motstand

$$R_L = 3,4 \text{ [\Omega]}$$

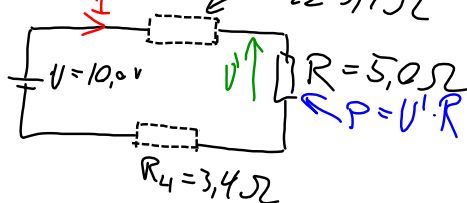Ekvivalent skjem a  $R_{L2} = 3,4 \Omega$ 

$$I = \frac{U}{R + 2R_L} = \frac{10,0 \text{ [V]}}{(5,0 + 2 \cdot 3,4) \text{ [\Omega]}} = \frac{10,0 \text{ [V]}}{11,8 \text{ [\Omega]}} = 0,84 \text{ [A]}$$

$$P = U' \cdot I = R \cdot I \cdot I = R \cdot I^2 = 5,0 \Omega \cdot 0,84^2 \text{ [A]} = 3,52 \text{ [W]}$$

Effekt i ledning

$$P_L = 2 \cdot R_L \cdot I^2 = 2 \cdot 3,4 \cdot 0,84^2 = 4,8 \text{ [W]}$$