

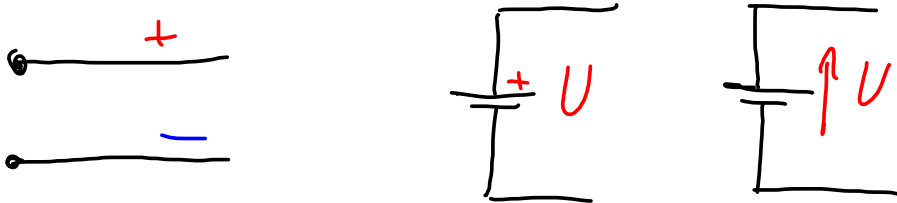


Likespenning

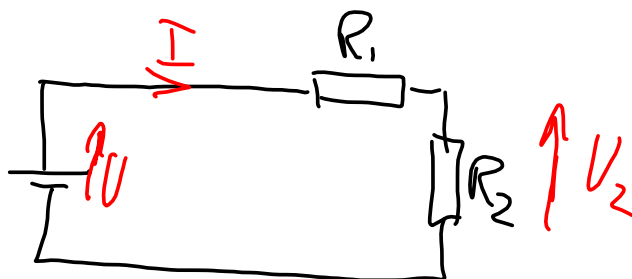


Ekse: $U = 10 \text{ [V]}$

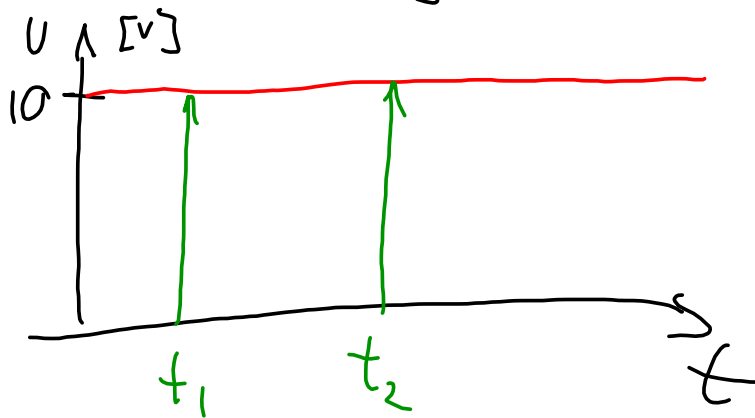


$$P = U \cdot I$$


$$P_{R2} = U_2 \cdot I = \frac{U_2^2}{R_2}$$

Veluskespenning

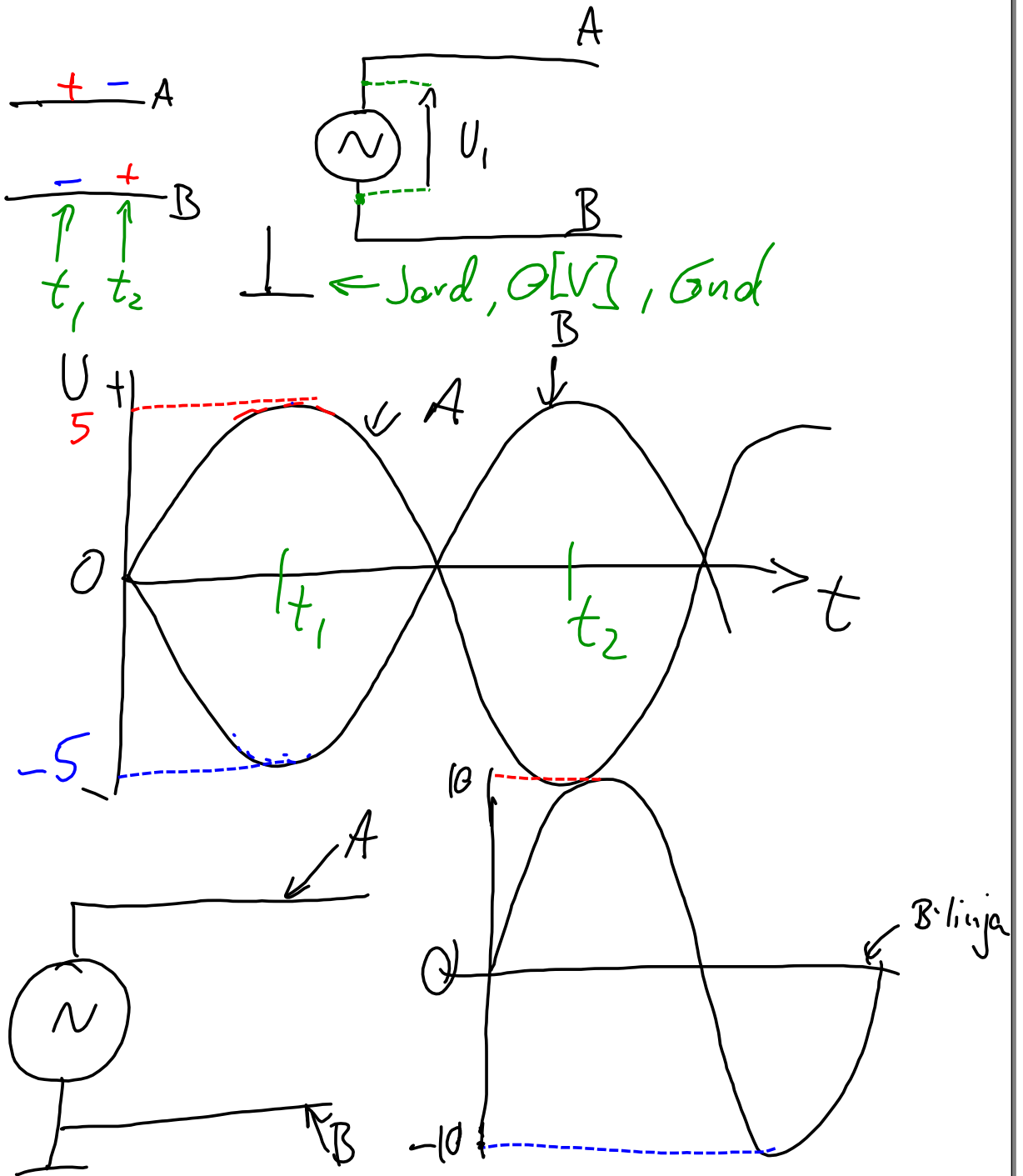

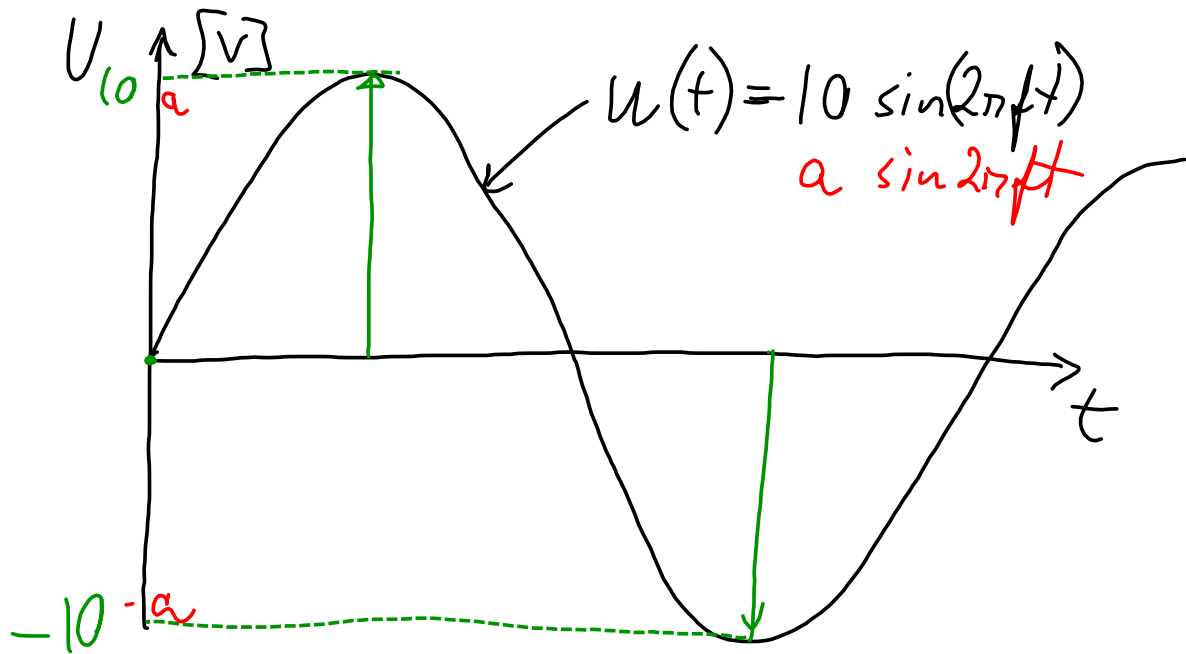


Vekselspanning

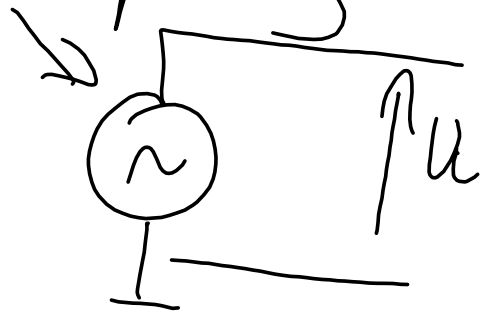

liten u
for vekselspanning

$P^?$

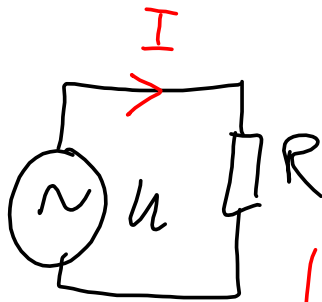


$u = R \cdot I$



$P = u \cdot i$



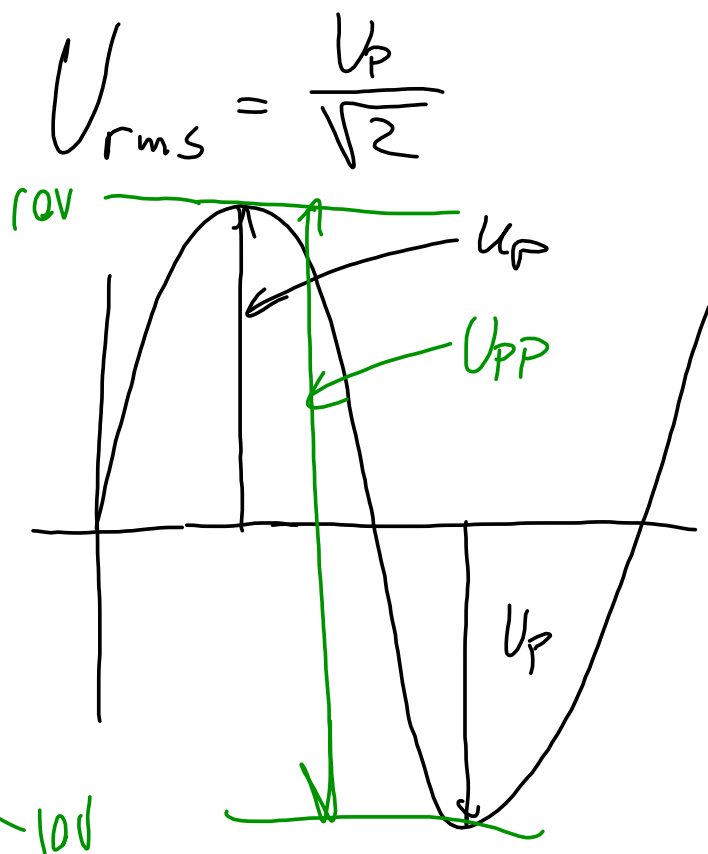

$$U_p = 10 \text{ V}$$

$$U_{pp} = 2 \cdot U_p = 20 \text{ V}$$

$$U_{rms} = \frac{10 \text{ V}}{\sqrt{2}} = 7,07 \text{ V}$$

Det er rms verdien som brukes
for å angi størrelsen på vekselspenning




$$I = \frac{U}{R} = \frac{7,1 [V]}{10 [\Omega]} = 0,71 [A]$$

$$P = 7,1 [V] \cdot 0,71 [A] = 5,0 [W]$$

\uparrow U_{rms} \uparrow I_{rms}

Et multimeter viser rms verdien

Et oscilloscop viser kurven $t(t)$ u

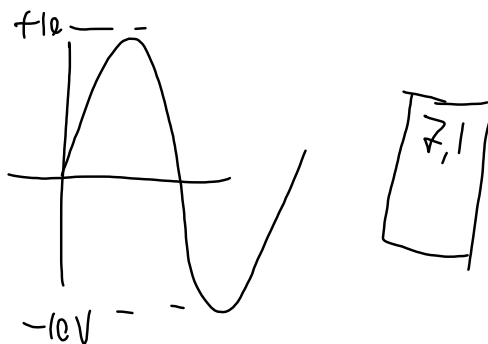



\leftarrow multimeteret

$$220 [V]$$

$$U_{\text{rms}} \cdot \sqrt{2} = U_p = 220V \cdot 1,4 = 311 V$$
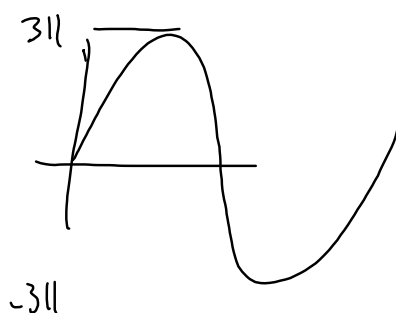
$$U_{\text{pp}} = 2 \cdot U_p = 2 \cdot 311 = 622 V$$



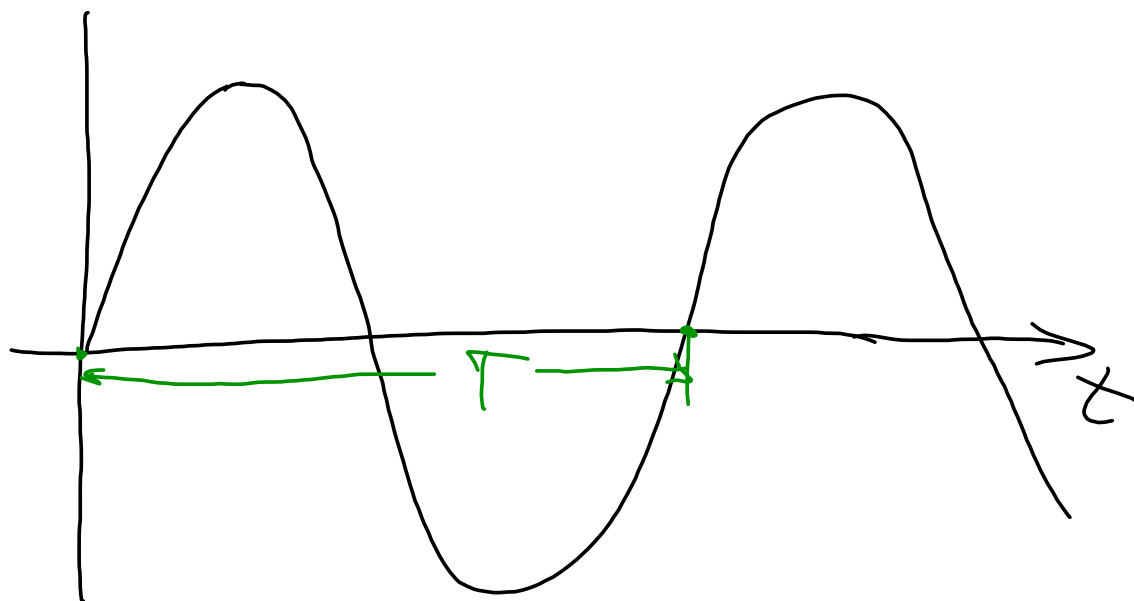

T : Periode


Periode

f : frekvens: $f = \frac{1}{T}$



$$\text{EKD: } T = 1,0 \text{ [ms]} = 1,0 \cdot 10^{-3} \text{ [s]}$$

$$f = \frac{1}{T} = \frac{1}{1,0 \cdot 10^{-3} \text{ [s]}} = 1,0 \cdot 10^3 \left[\frac{1}{\text{s}} \right]$$
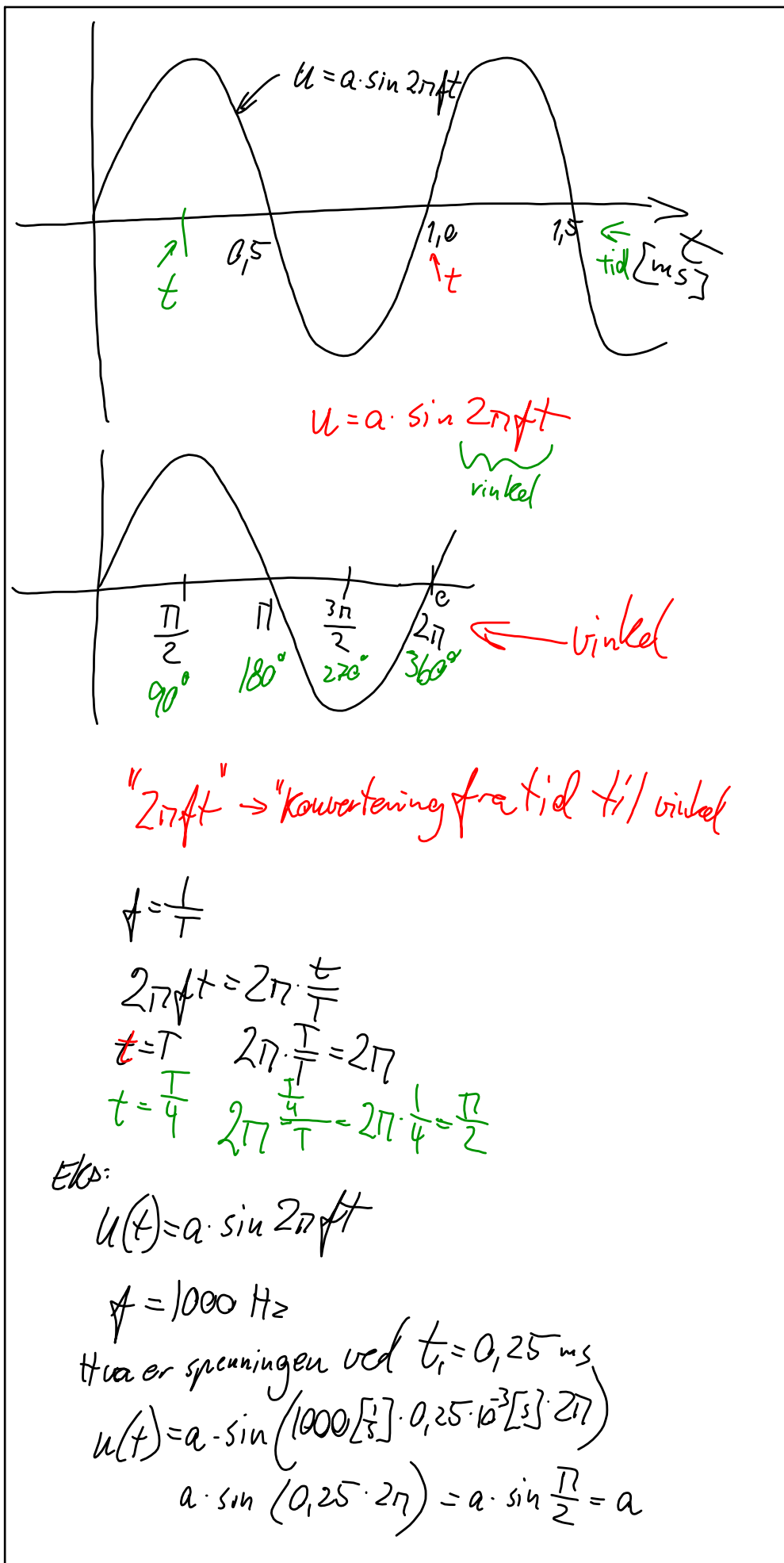
$$= 1000 \text{ [Hz]} = 1,0 \text{ kHz} \quad \downarrow \text{ Hz}$$



Faseforskyvning

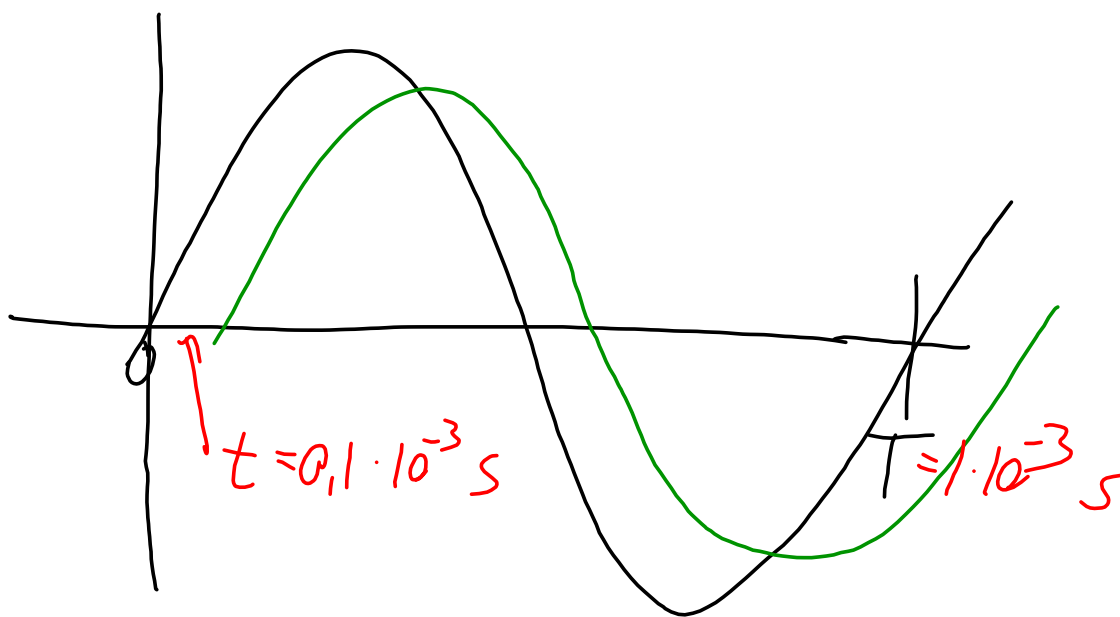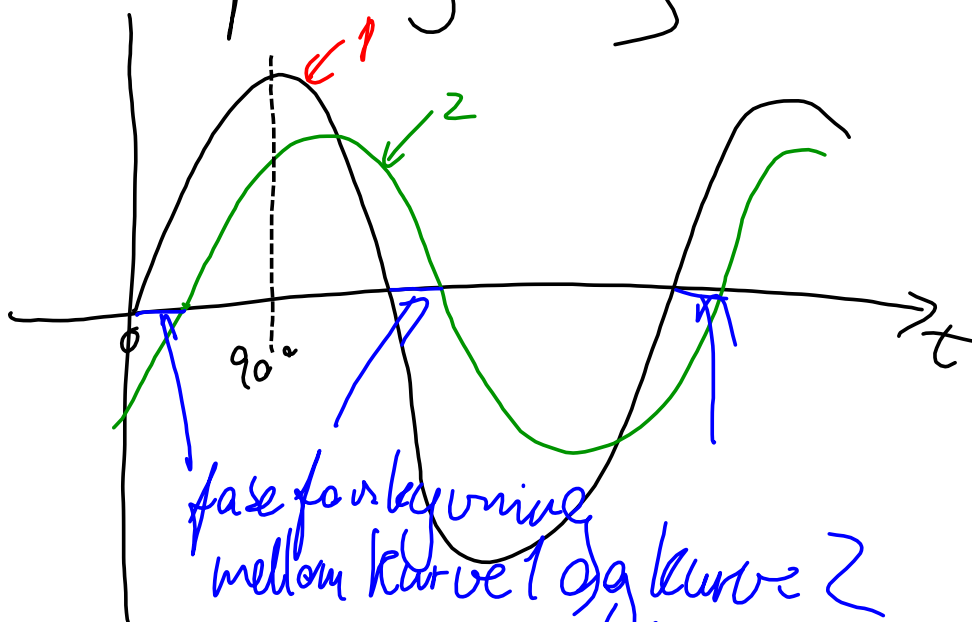

$$T = \frac{1}{f} = \frac{1}{1000 [\text{Hz}]} = 1 \cdot 10^{-3} [\text{s}]$$

$$\frac{t}{T} \cdot 360^\circ = \frac{0,1 \cdot 10^{-3}}{1,0 \cdot 10^{-3}} \cdot 360^\circ = 0,1 \cdot 360^\circ = \underline{36^\circ}$$

Ubalansert \leftrightarrow Balansert

