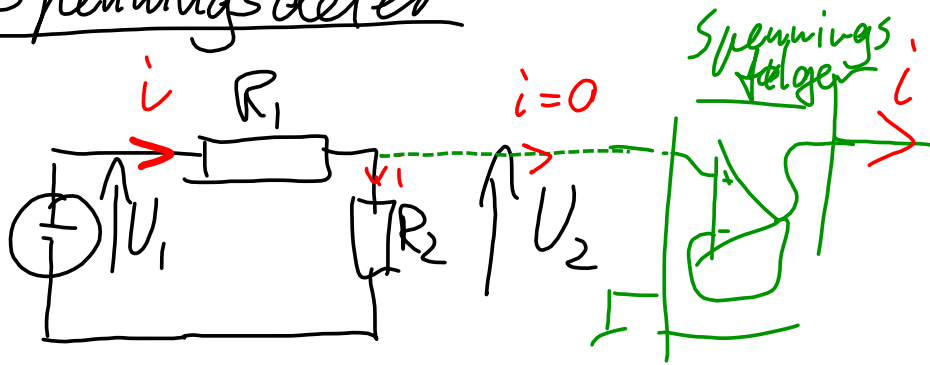


# Spenningsdeler



$$i = \frac{U_1}{R_1 + R_2} \quad U_2 = i \cdot R_2$$

$$U_2 = \frac{U_1}{R_1 + R_2} \cdot R_2$$

$$\frac{U_2}{U_1} = \frac{R_2}{R_1 + R_2}$$

Eks  $\frac{U_2}{U_1} = 0,2 = \frac{R_2}{R_1 + R_2}$

$$0,2 \cdot R_1 + 0,2 \cdot R_2 = R_2$$


$$0,2 \cdot R_1 = R_2 - 0,2 R_2 = 0,8 R_2$$

$$R_1 = \frac{0,8 R_2}{0,2} = 4,0 \cdot R_2$$

Velger  $\rightarrow R_2 = 1,5 \text{ k}\Omega$

$$R_1 = 4,0 \cdot 1,5 \text{ k}\Omega = 6,0 \text{ k}\Omega$$

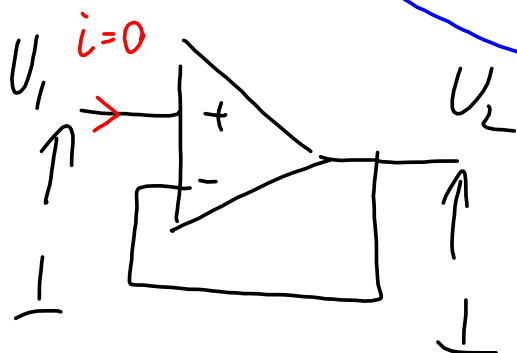Spenningsfølger  $\Rightarrow \frac{U_2}{U_1} = 1 \quad U_2 = U_1$



$$i = \frac{U_2}{R_2 + R_1} \quad U_1 = i \cdot R_1$$


$$U_1 = \frac{U_2}{R_2 + R_1} \cdot R_1$$


$$\frac{U_2}{U_1} = \frac{R_2 + R_1}{R_1} = 1 + \frac{R_2}{R_1}$$

$$R_2 = 0$$

$$R_1 = \infty$$
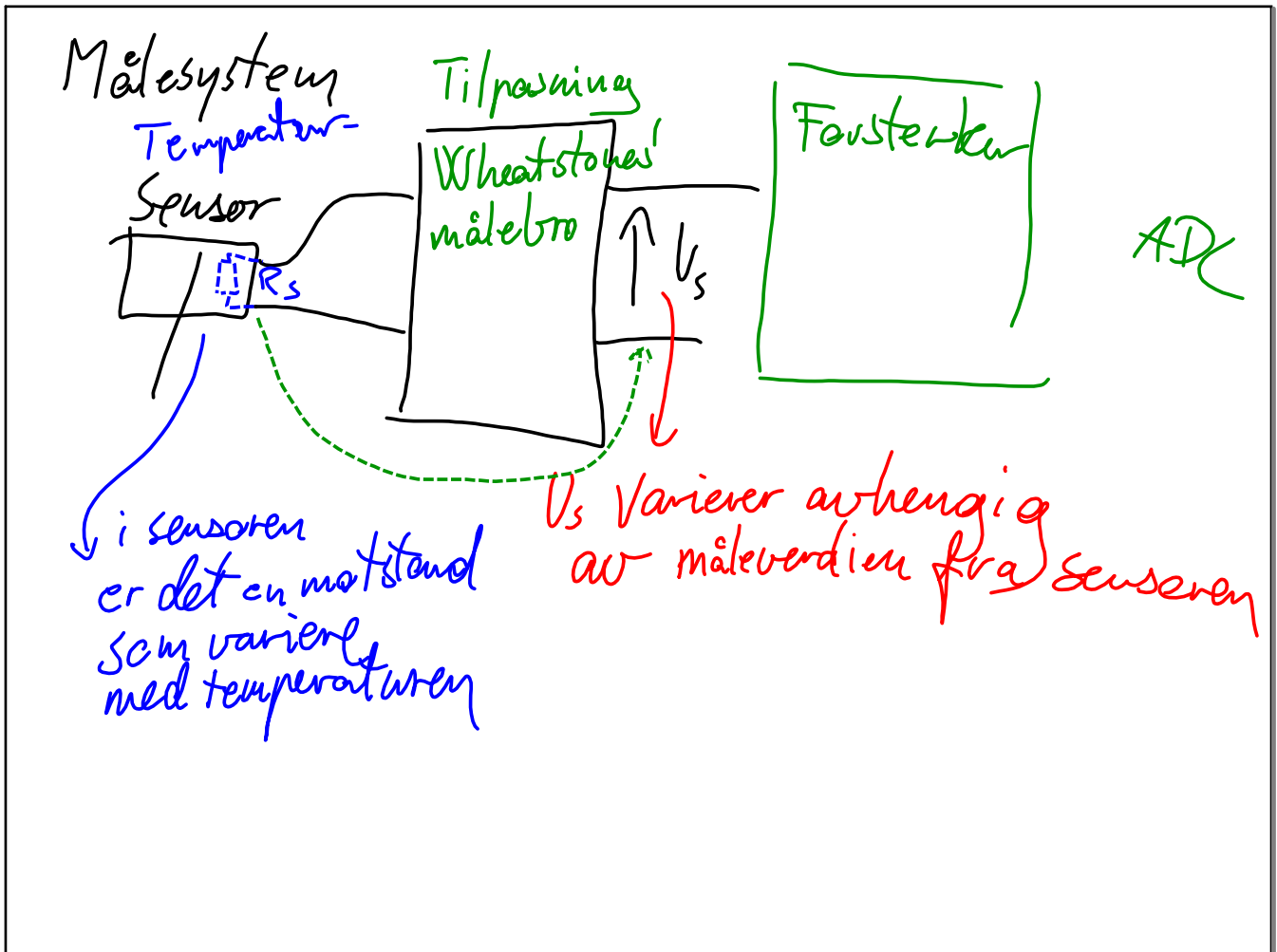
$$\frac{U_2}{U_1} = 1 + \frac{0}{\infty} = 1$$



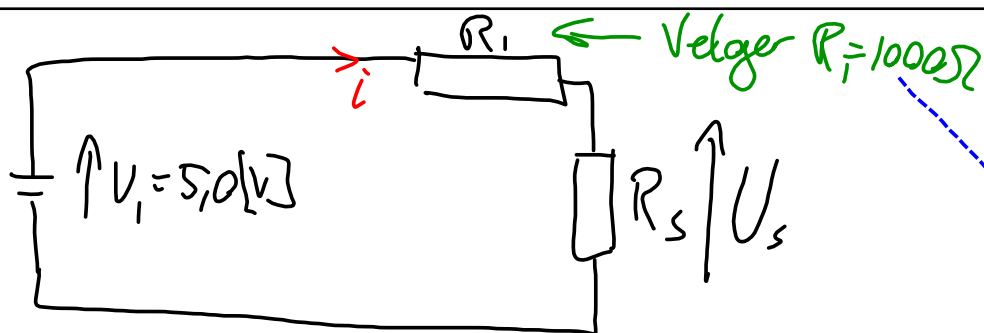

$R_s$  er en Pt1000 temperatur sensor

$$-10^\circ \text{C} \Rightarrow +20^\circ \text{C}$$

$$R_s = 960,9 \Omega \quad R_s = 1077,9 \Omega$$

$$i = \frac{U_1}{R_1 + R_s} \quad U_s = i \cdot R_s$$

$$U_s = \frac{U_1}{R_1 + R_s} \cdot R_s$$

$$\frac{U_s}{U_1} = \frac{R_s}{R_1 + R_s}$$


$$U_s = \frac{R_s}{R_1 + R_s} \cdot U_1$$

Hva er  $U_s$  ved  $t = -10^\circ \text{C}$

$$U_s = \frac{960,9}{1000 + 960,9} \cdot 5,0 \text{ [V]} = 2,45 \text{ V}$$

Hva er  $U_s$  ved  $t = +20,0^\circ \text{C}$
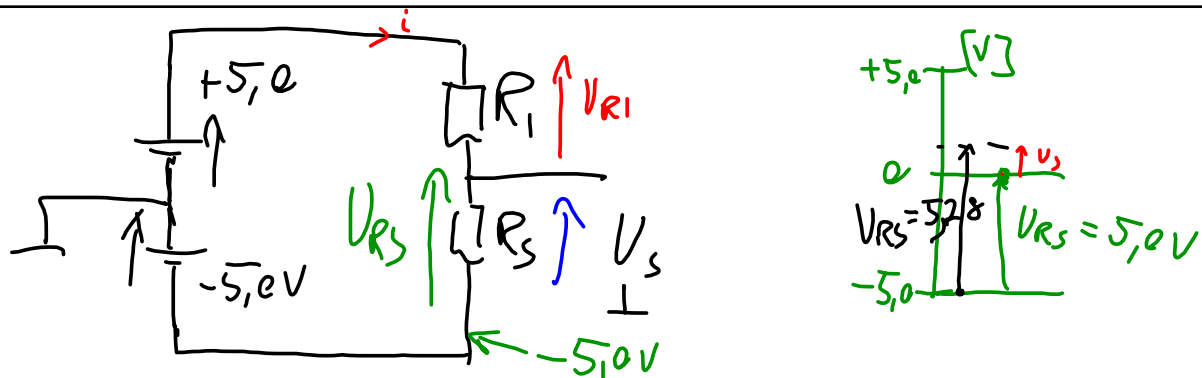
$$U_s = \frac{1077,9}{1000 + 1077,9} \cdot 5,0 \text{ [V]} = 2,59 \text{ [V]}$$




Vi ønsker at  $V_s = 0,0\text{V}$  ved  $-20,0^\circ\text{C}$   
 Da må  $R_1 = R_s = 960,9\ \Omega$   
 ved  $-10^\circ\text{C}$

$$V_{RS} = \frac{10\text{V}}{R_1 + R_s} \cdot R_s = 10[\text{V}] \cdot \frac{960,9}{2 \cdot 960,9} = \frac{10}{2} = 5,0\text{V}$$


Hva er  $V_s$  ved  $+20^\circ\text{C}$

$$V_{RS} = \frac{10,0[\text{V}]}{R_1 + R_s} \cdot R_s = 10,0[\text{V}] \cdot \frac{1077,9}{960,9 + 1077,9} = 5,28[\text{V}]$$
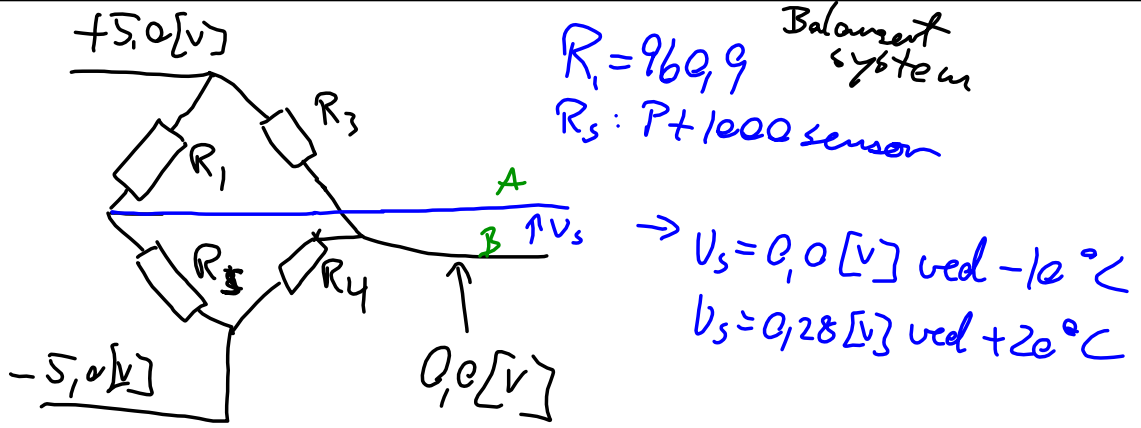
$$V_s = V_{RS} - 5,0[\text{V}] = 5,28[\text{V}] - 5,0[\text{V}] = \underline{\underline{0,28\text{V}}}$$



$R_3 = R_4 = 1000 \Omega$

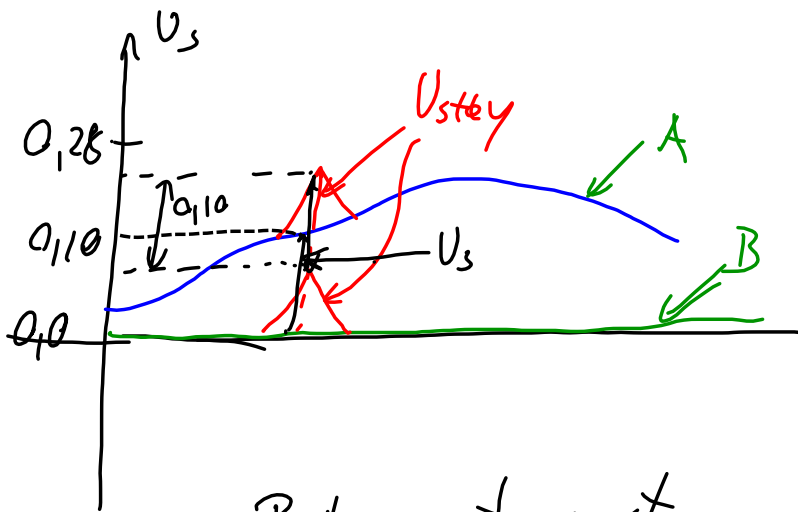

Balansert system  
Balansert forsterker

