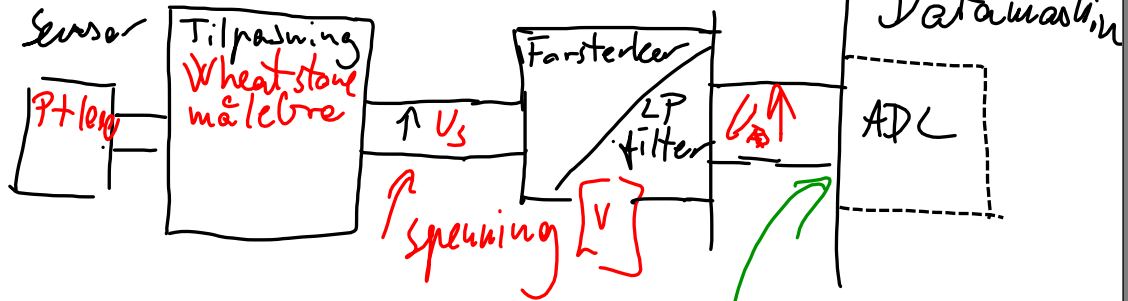


# Et balansert målesystem

↳ Temperatur måler

Pt 1000 temp sensor




Bestemme temp område

-40,0°C → +40,0°C

Hvor mange bit bør ADC ha?

→ 8 bit : FSR : 5,0V
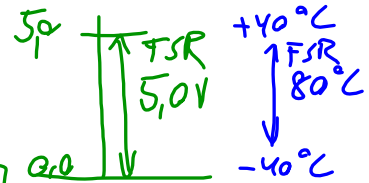
$$1 \text{ LSB} = \frac{\text{FSR}}{2^n - 1} = \frac{5,0\text{V}}{2^8 - 1} = 0,019\text{V}$$



$$1 \text{ LSB} = \frac{80^\circ\text{C}}{2^8 - 1} = 0,31^\circ\text{C}$$


Kvantiseringsfeil ± 1/2 LSB

$$\frac{0,31}{2} = 0,15 \Rightarrow \pm 0,15^\circ\text{C}$$

LP-filter:

Grensefrekvens: 100 Hz →  $f_s \gg 10 \cdot f_s$

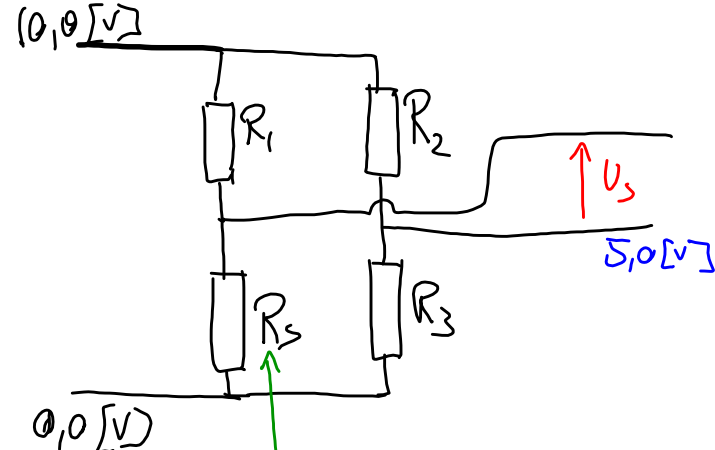Hva er høyeste frekvens i temp. signalet  $f_s = 10 \text{ Hz}$




$10,0 [V]$   
 $0,0 [V]$   
 $5,0 [V]$   
 $U_s$   
 $R_1$   
 $R_2$   
 $R_3$   
 $R_5$

$P+1000$   
 $-40,0^\circ C \Rightarrow R_5 = 842,70 \Omega$   
 $+40,0^\circ C \Rightarrow R_5 = 1155,40 \Omega$

$U_s = 0,0 [V]$  ved  $-40,0^\circ C$   
 Da må  $R_1 = R_5 = 842,70 \Omega$   
 $\uparrow$  ved  $-40^\circ C$

$R_3 = R_4$  for at ref. spenning er  $5,0 [V]$   
 $R_3 // R_4 \approx R_1 // R_5$   $R_3 = R_4 = 842,70 \Omega$

Hva er  $U_s$  ved  $+40,0^\circ C$  ?

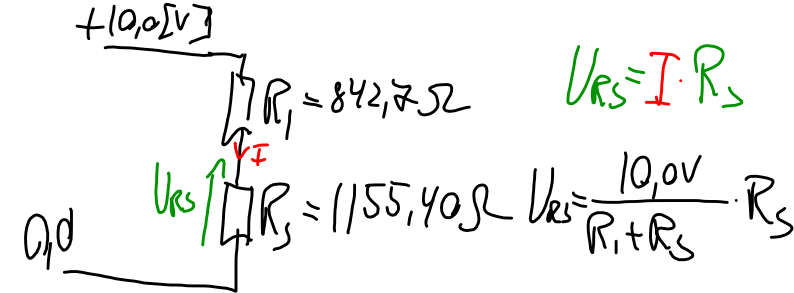


$+10,0 [V]$   
 $R_1 = 842,7 \Omega$   
 $R_5 = 1155,40 \Omega$   
 $U_{R5} = I \cdot R_5$   
 $U_{R5} = \frac{10,0V}{R_1 + R_5} \cdot R_5$

$U_{R5} = \frac{10,0 [V] \cdot 1155,40}{842,70 + 1155,40} = 5,78 [V]$

$U_s = U_{R5} - 5,0 [V] = 5,78 - 5,0 = 0,78 [V]$

$U_s = 0,0 [V]$   $-40,0^\circ$   $U_s = 0,78 [V]$   $+40^\circ C$

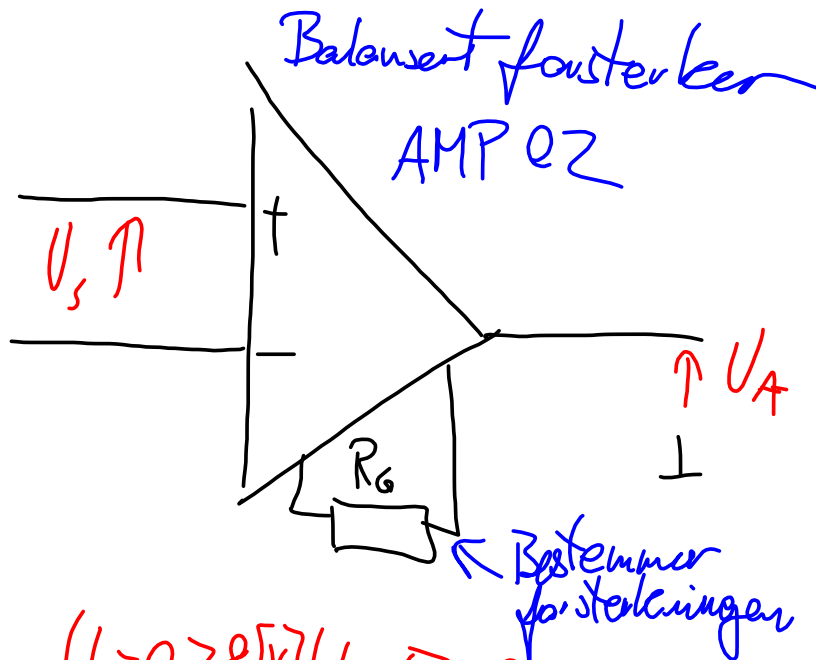Vi må bestemme forsterkningen i forsterkeren



$$U_s = 0,78 [V] \quad U_A = 5,0 [V]$$

$$U_s = 0,0 [V] \quad U_A = 0,0 [V]$$


$$0,78 \cdot G = 5,0$$

$$G = \frac{5,0}{0,78} = 6,4 [gg] = \frac{50K\Omega}{R_G} + 1$$

$$6,4 - 1 = \frac{50K}{R_G} = 5,4$$

$$R_G = \frac{50K}{5,4} = \underline{\underline{9,3 K\Omega}}$$

LP-filter

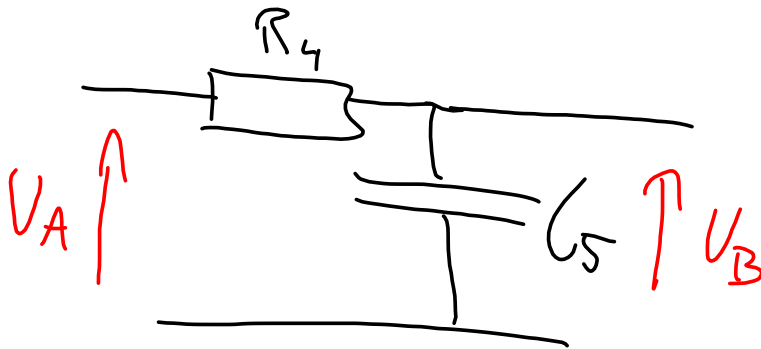

$$f_G = \frac{1}{2\pi R_4 C_5} = 100 \text{ [Hz]}$$


↑  
Velger

$$R_4 = \frac{1}{2\pi \cdot 100 \cdot C_5} = \frac{1}{2\pi \cdot 100 \cdot 220 \cdot 10^{-9}}$$


↑  
 $f_G$

↑  
 $220 \mu\text{F}$

$$= 7234 \Omega$$

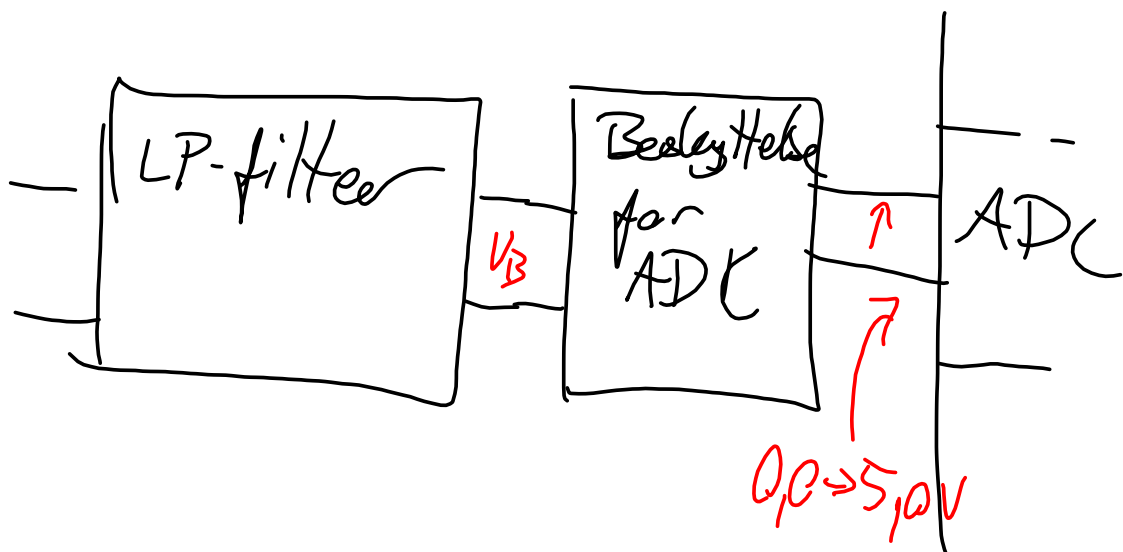


Ubalansert

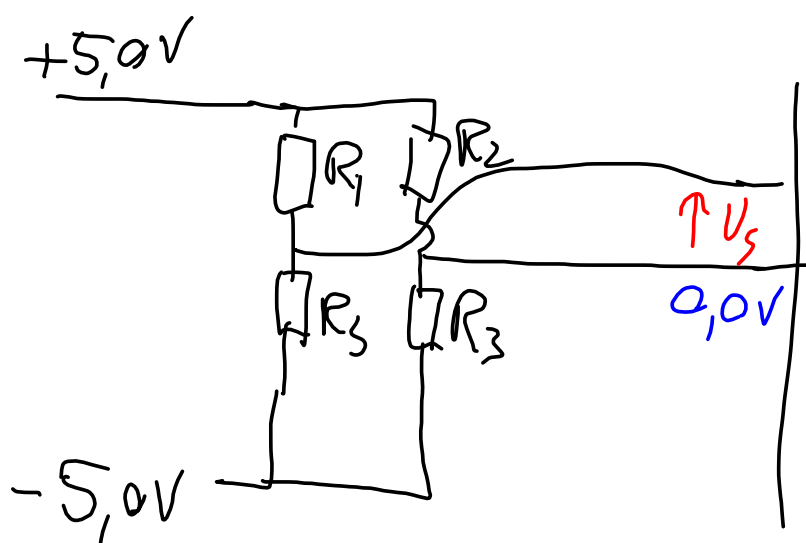

Ubalansert  
faste deler

# Ubalansert Forsterker

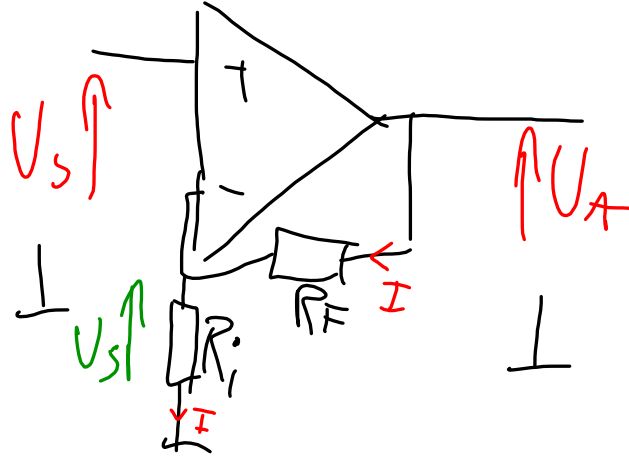

Forsterkning på 6,4

$$\left( \frac{U_A}{R_F + R_i} \right) \cdot R_i = U_s$$

$$\frac{U_A}{U_s} = \frac{R_F + R_i}{R_i} = 1 + \frac{R_F}{R_i} = 6,4$$

$$\frac{R_F}{R_i} = 6,4 - 1 = 5,4$$

$$R_F = 5,4 \cdot R_i$$

↑  
Velger 1,2K

$$= 5,4 \cdot 1,2K = 6,5K\Omega$$

