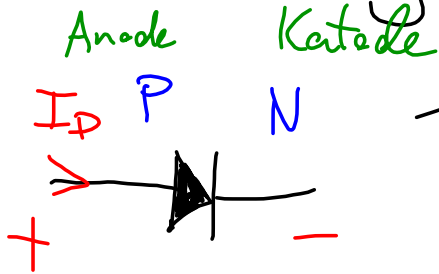


Dioden

PN-overgang




Leeder strøm


$V_D = 0,7\text{ V}$

(Si dioder)

Ge -||- $V_D = 0,2\text{ V}$


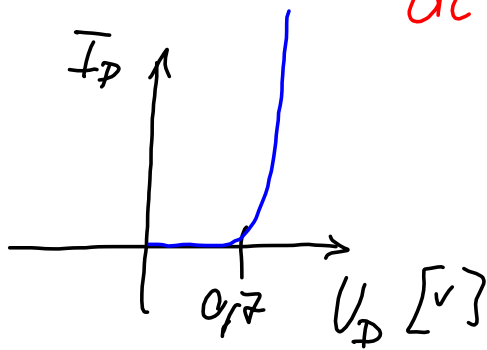


Digitalt signal

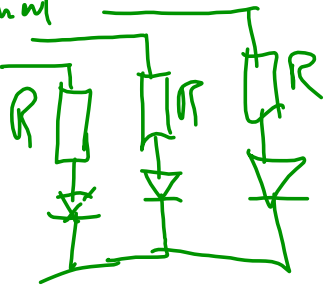

Felles katode

Syv segment

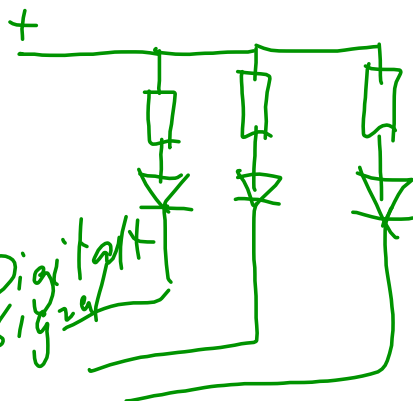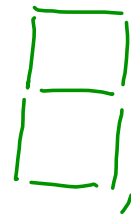

Felles anode

Likentter

