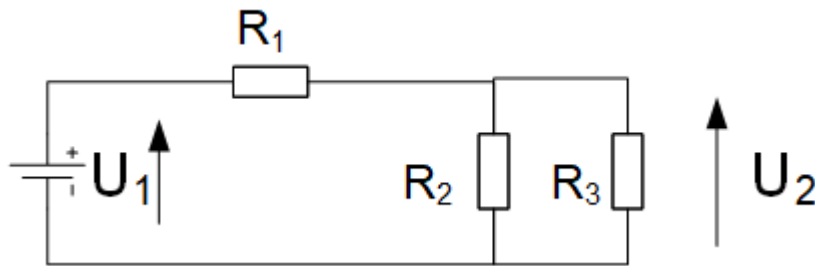


I kretsen til venstre er $U_1 = 5,0$ [V], $R_1 = 1500$ [Ω] og $R_2 = 2000$ [Ω]

Hvor stor er strømmen I , og spenningen U_2 .

$$I = \frac{U_1}{(R_1 + R_2)} = \frac{5,0 \text{ [V]}}{(1500 + 2000) \text{ [\Omega]}} = 0,00143 \text{ [A]} = 1,43 \cdot 10^{-3} \text{ [A]} = 1,43 \text{ [mA]}$$


$$U_2 = I \cdot R_2 = 1,43 \cdot 10^{-3} \cdot 2000 \text{ [A} \cdot \Omega] = 2,86 \text{ [V]}$$



I Kretsen til venstre er $U_1 = 10,0$ [V], $R_1 = 1000$ [Ω], $R_2 = R_3 = 2000$ [Ω]

Hvor stor er spenningen U_2 .

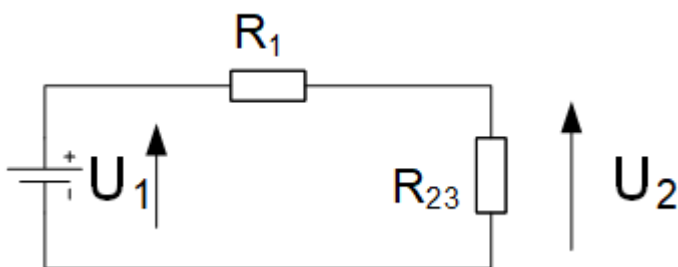Lager et ekvivalentskjema, hvor R_{23} er parallell-koblingen av R_2 og R_3 .



$$R_{23} = \frac{R_2 \cdot R_3}{R_2 + R_3} = \frac{2000 \text{ [\Omega]} \cdot 2000 \text{ [\Omega]}}{2000 \text{ [\Omega]} + 2000 \text{ [\Omega]}} = \frac{4000000}{4000} \text{ [\Omega]} = 1000 \text{ [\Omega]}$$

$$U_2 = I \cdot R_{23} = \frac{U_1}{(R_1 + R_{23})} \cdot R_{23} = \frac{10,0 \text{ [V]}}{(1000 + 1000) \text{ [\Omega]}} \cdot 1000 \text{ [\Omega]} = 5,0 \text{ [V]}$$